



To simulate Operational Amplifiers, use “UniversalOpamp2”.  $V_{CC} = +15V$  and  $V_{EE} = -15V$

To simulate Zener Diodes, use “1N750” 4.7V Zener Diode.

### Experiment 5.1.

Simulate the circuit shown in Figure-1.

**Outputs:** Plot the output voltage ( $V_{o-t}$ ) and input voltage ( $V_{i-t}$ ) for two different reference voltage ( $V_{ref}$ ).

Explain the circuit and simulation results.

**Note:** You can use two resistors, instead of potentiometer. The sum of the resistor values should be 10K.

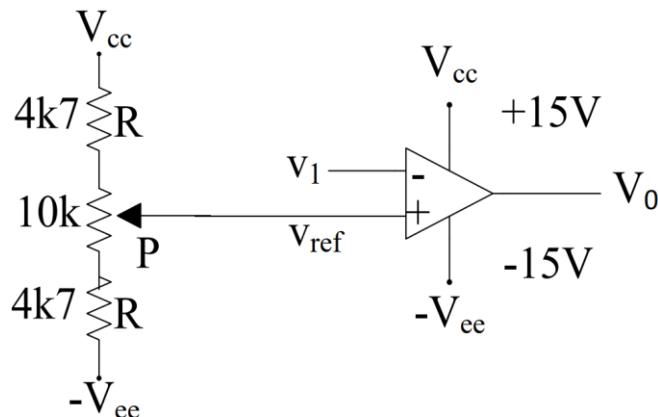


Figure 1: Voltage comparator test circuit.

Table 1: Input Signal Parameters ( $V_1$ ) for Experiment 5.1.

| Exp 5.1 - $V_1$ |                           |
|-----------------|---------------------------|
| Type            | Triangle                  |
| Frequency       | 100Hz                     |
| Amplitude       | 10V (20V <sub>p-p</sub> ) |
| DC Offset       | 0V                        |

### Experiment 5.2.

Simulate the circuit shown in Figure-2.

**Outputs:** Plot the output voltage of the OPAMP ( $V_0 - t$ ), output voltage of the circuit ( $V_0' - t$ ) and input voltage ( $V_1 - t$ ).

Explain the circuit and simulation results.

**Note:**  $V_{ref}$  should be grounded. The zener voltage of the diodes is 4.7V.

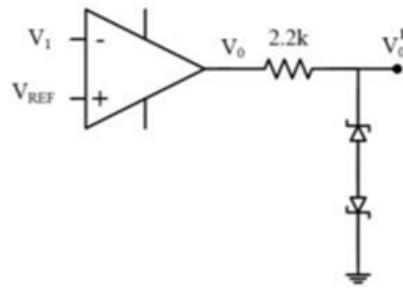


Figure 2: Voltage limiter circuit.

Table 2: Input Signal Parameters ( $V_1$ ) for Experiment 5.2.

| Exp 5.2 - $V_1$ |                           |
|-----------------|---------------------------|
| Type            | Triangle                  |
| Frequency       | 100Hz                     |
| Amplitude       | 10V (20V <sub>p-p</sub> ) |
| DC Offset       | 0V                        |

**Experiment 5.3. and Experiment 5.4.**

Simulate the circuit shown in Figure-3.

**Outputs:** Plot the output voltage ( $V_0 - t$ ) and input voltage ( $V_1 - t$ ) graphs.

Find the hysteresis parameters  $V_{01}$ ,  $V_{02}$ ,  $V_{11}$  and  $V_{12}$  as shown in Figure 4.

Explain the circuit and simulation results.

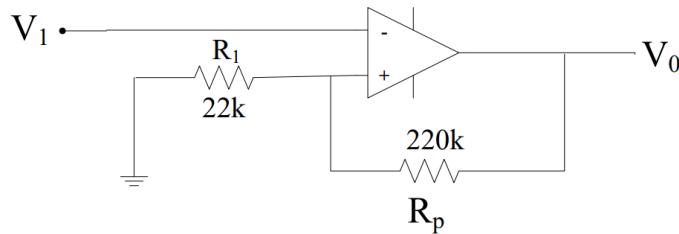


Figure 3: Schmitt trigger circuit.

Table 3: Input Signal Parameters ( $V_1$ ) for Experiment 5.3 and Experiment 5.4.

| Exp 5.3-5.4. - $V_1$ |                           |
|----------------------|---------------------------|
| Type                 | Triangle                  |
| Frequency            | 100Hz                     |
| Amplitude            | 10V (20V <sub>p-p</sub> ) |
| DC Offset            | 0V                        |

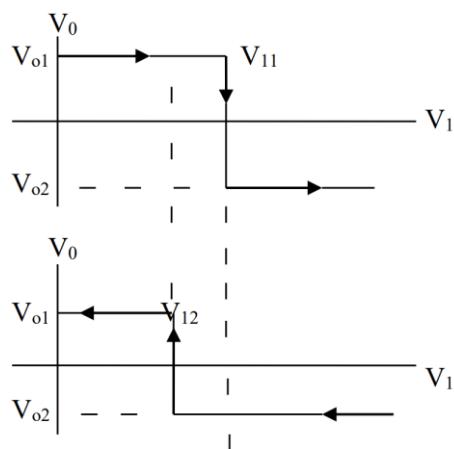


Figure 4: Hysteresis characteristic.

### Experiment 5.5.

Simulate the circuit shown in Figure-5. Find the potentiometer resistance value for the symmetric output voltage waveform.

**Outputs:** Plot the output voltage ( $V_o - t$ ), input voltage ( $V_i - t$ ) and ( $V_o' - t$ )

Explain the circuit and simulation results.

**Note:** The zener voltage of the diodes is 4.7V.

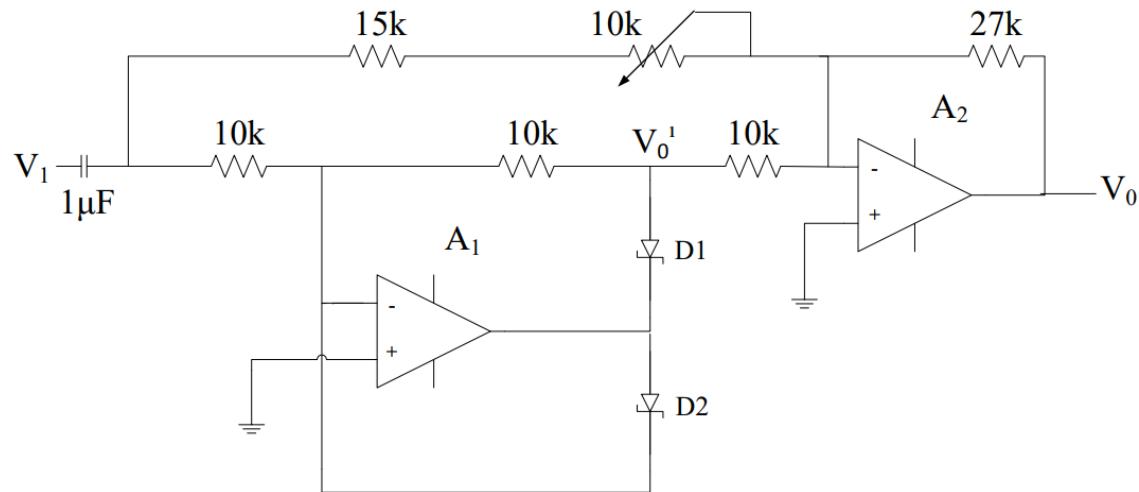


Figure 5: Full-wave rectifier circuit.

Table 4: Input Signal Parameters ( $V_1$ ) for Experiment 5.5.

| Exp 5.5. - $V_1$ |                   |
|------------------|-------------------|
| Type             | Sine              |
| Frequency        | 1kHz              |
| Amplitude        | Appropriate Level |
| DC Offset        | 0V                |